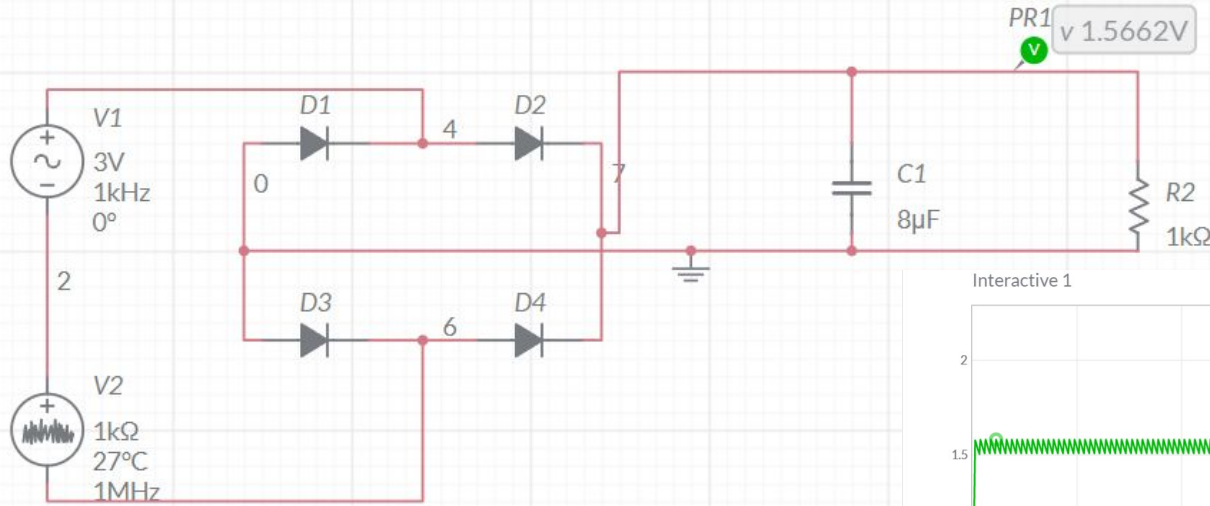



Circuit Design for Electromagnetic Energy Harvesting  
Mayukhmali Das
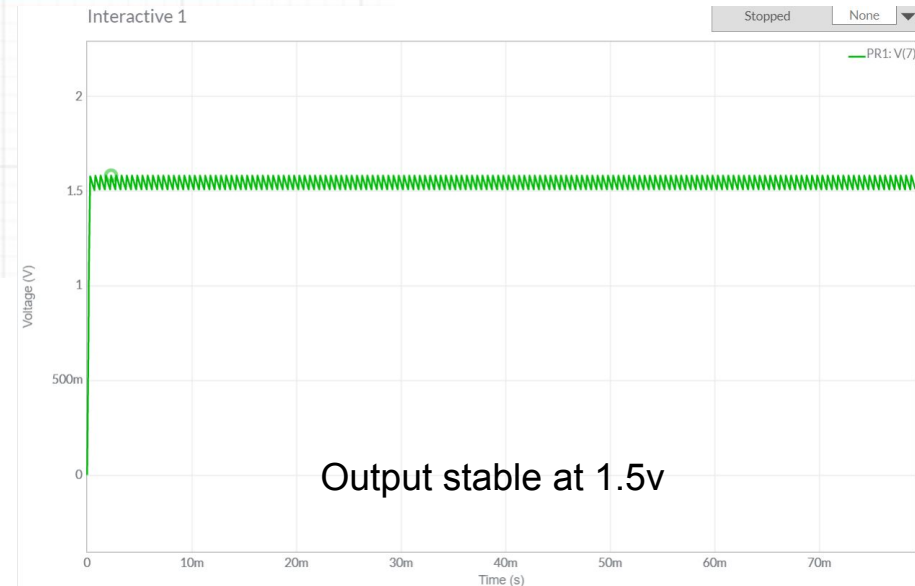
## Simple EMEH Circuit Design


We model the EMEH as a noisy sinusoid. We will choose the resistance and inductance value to match with the impedance of the EMEH for maximum power transfer *However the method of impedance matching is old and has low conversion efficiency*




Rectifier converts AC to DC. The capacitive filter is used to filter out the noise.



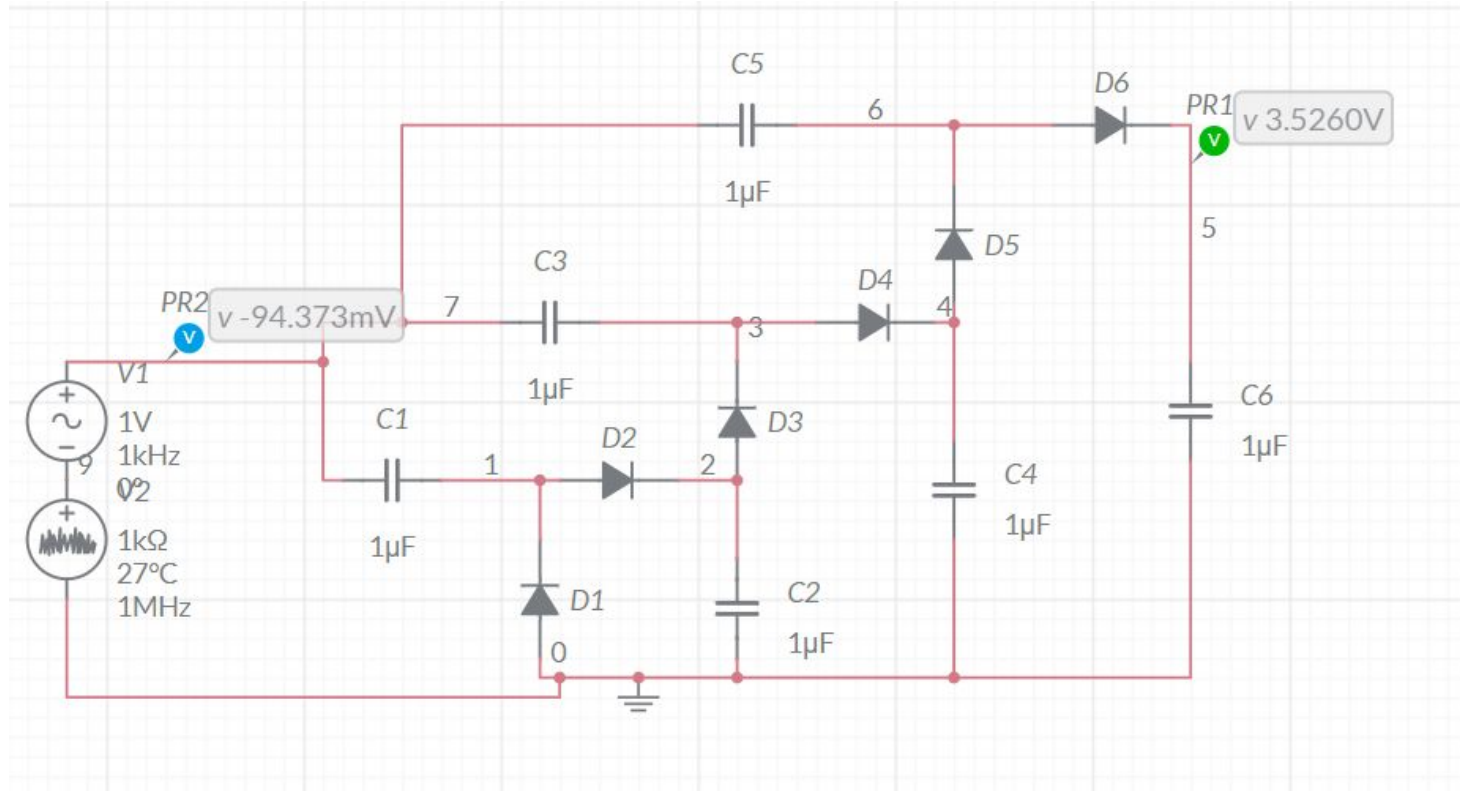In some studies I came across n stage rectifiers are used




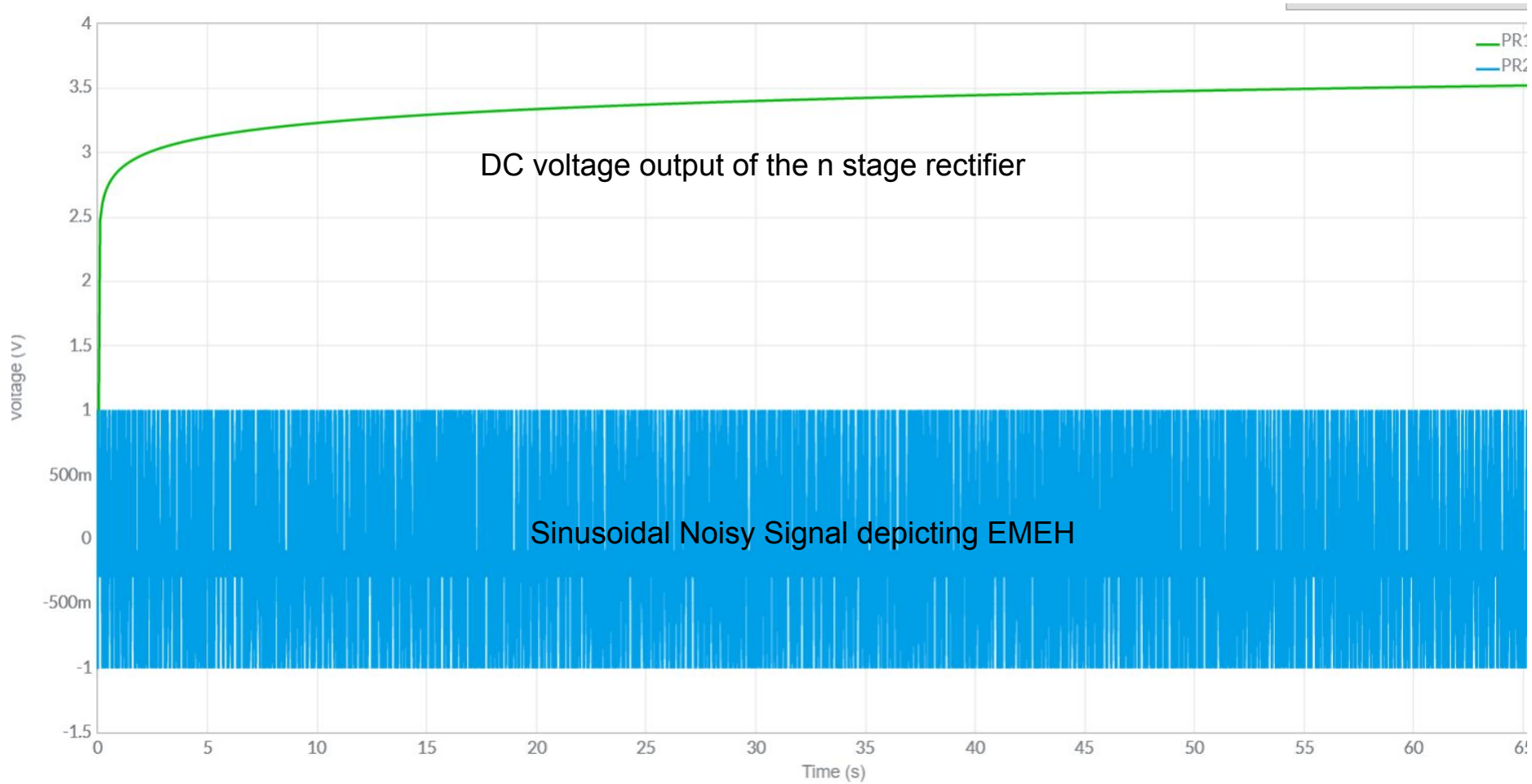


## **Buck Boost Converter Design**


***Synchronous switch harvesting  
on inductor (SSH) technique***
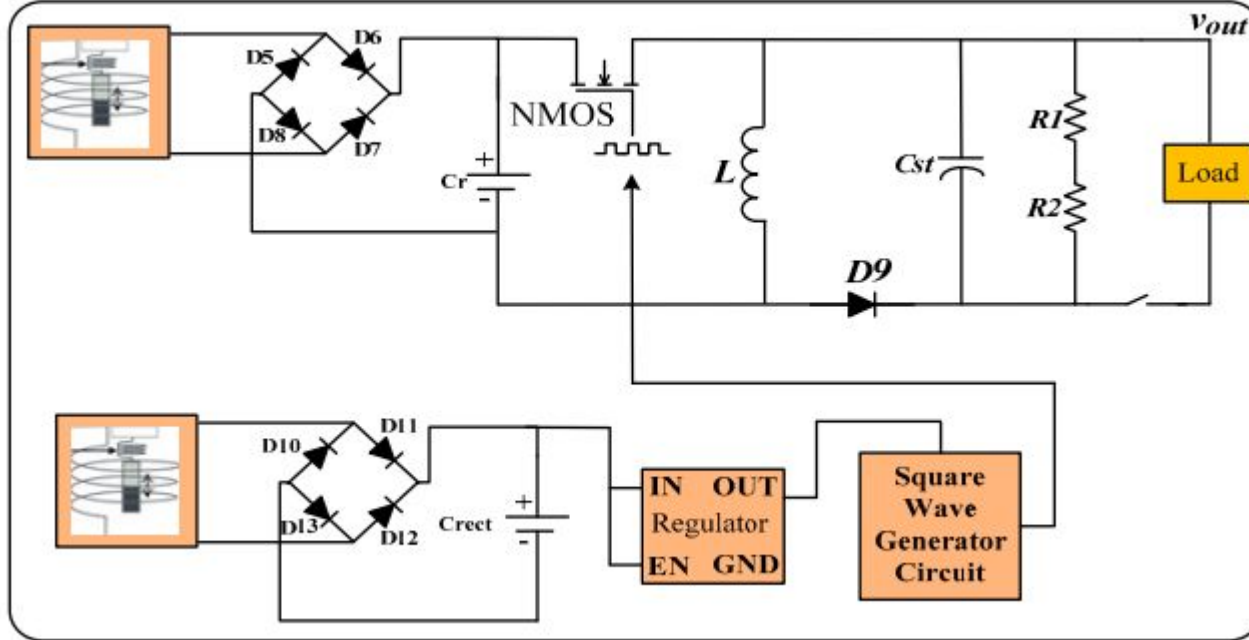
## *Synchronous switch harvesting on inductor (SSH) technique*




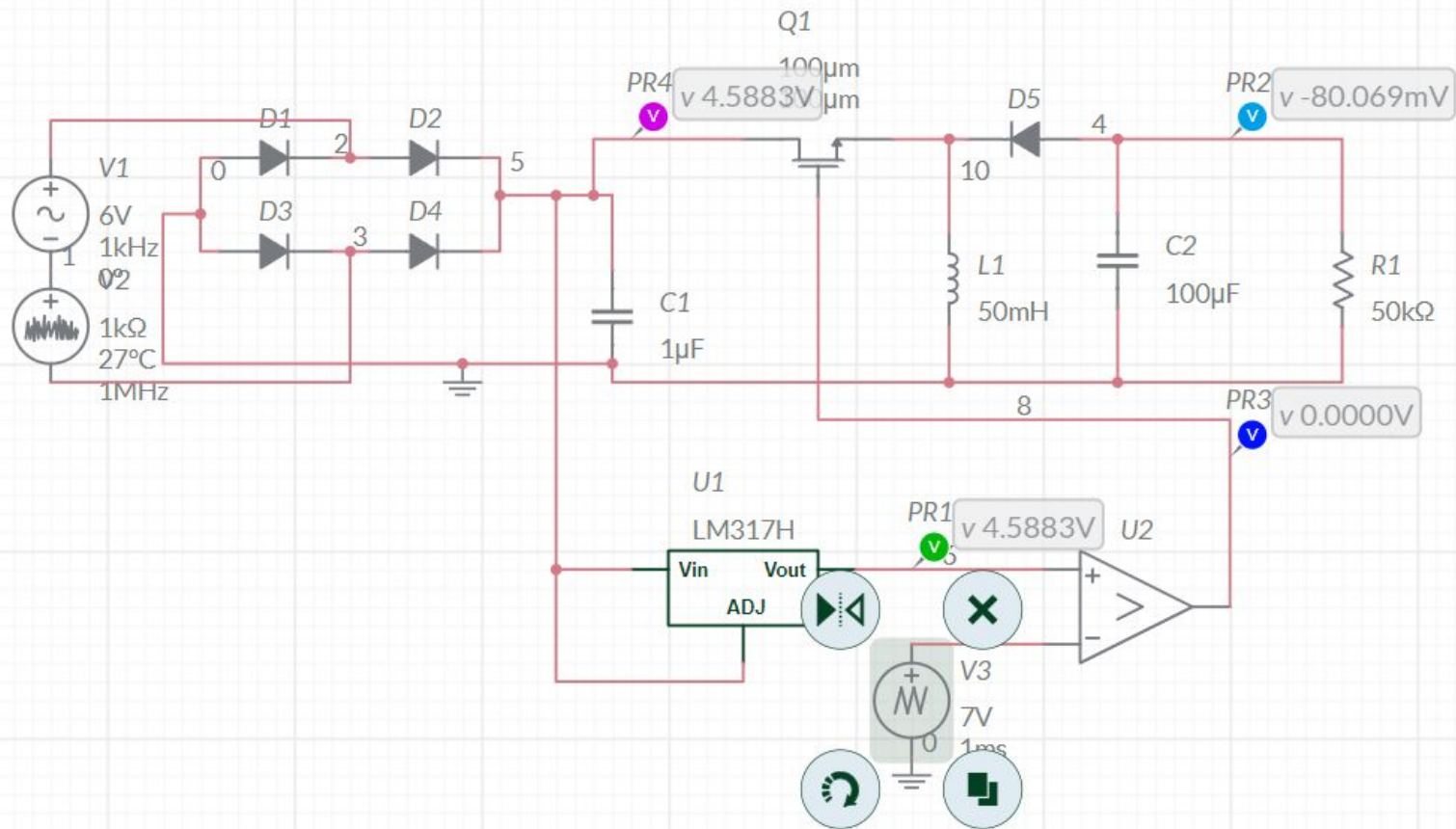



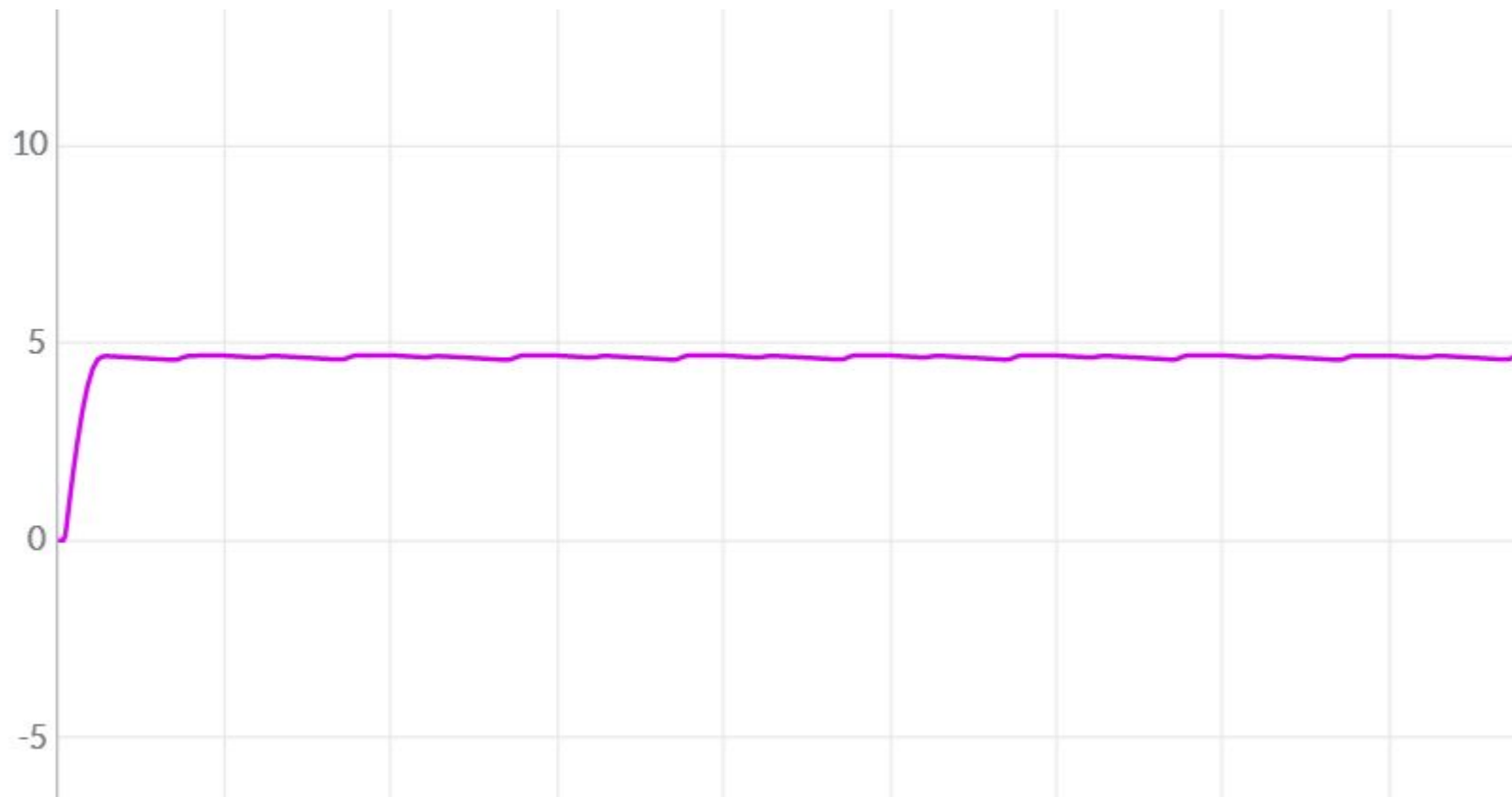


Voltage after rectification

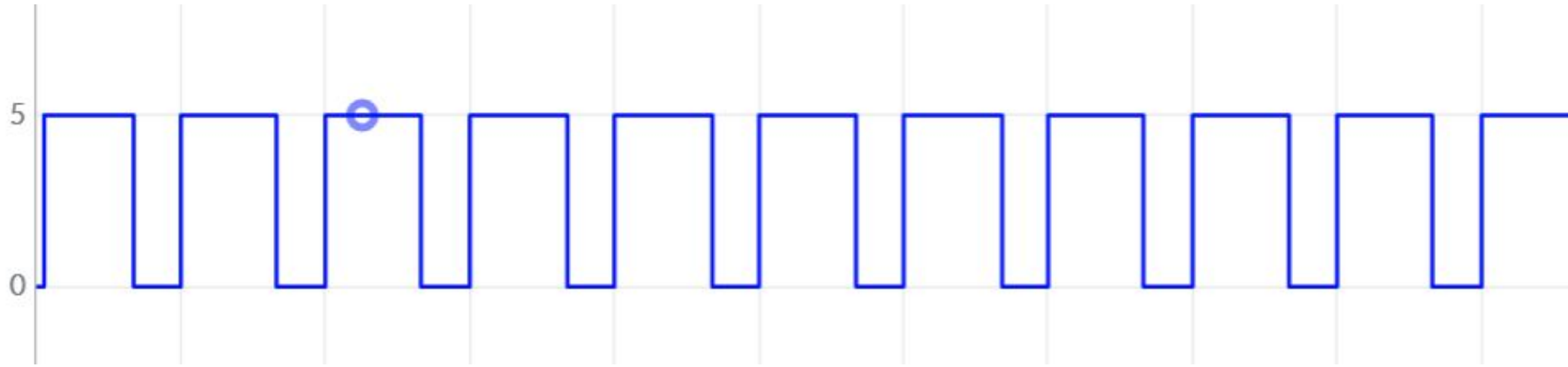


This is the PWM generated using the saw tooth wave and the rectified signal as reference.

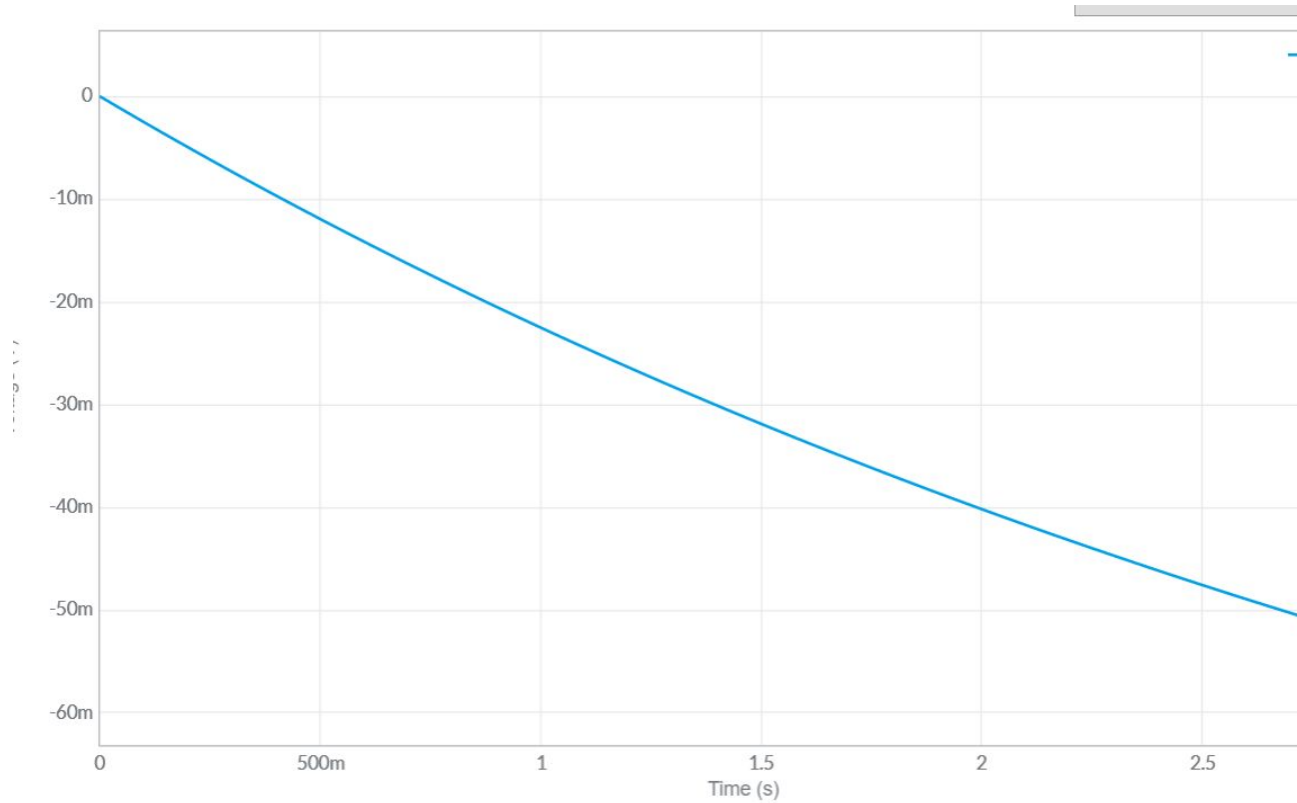Buck Boost Converters have inverted output voltage. The simulation output looks like this :




## Boost Converter Circuit

## Boost Converter Circuit for EMEH

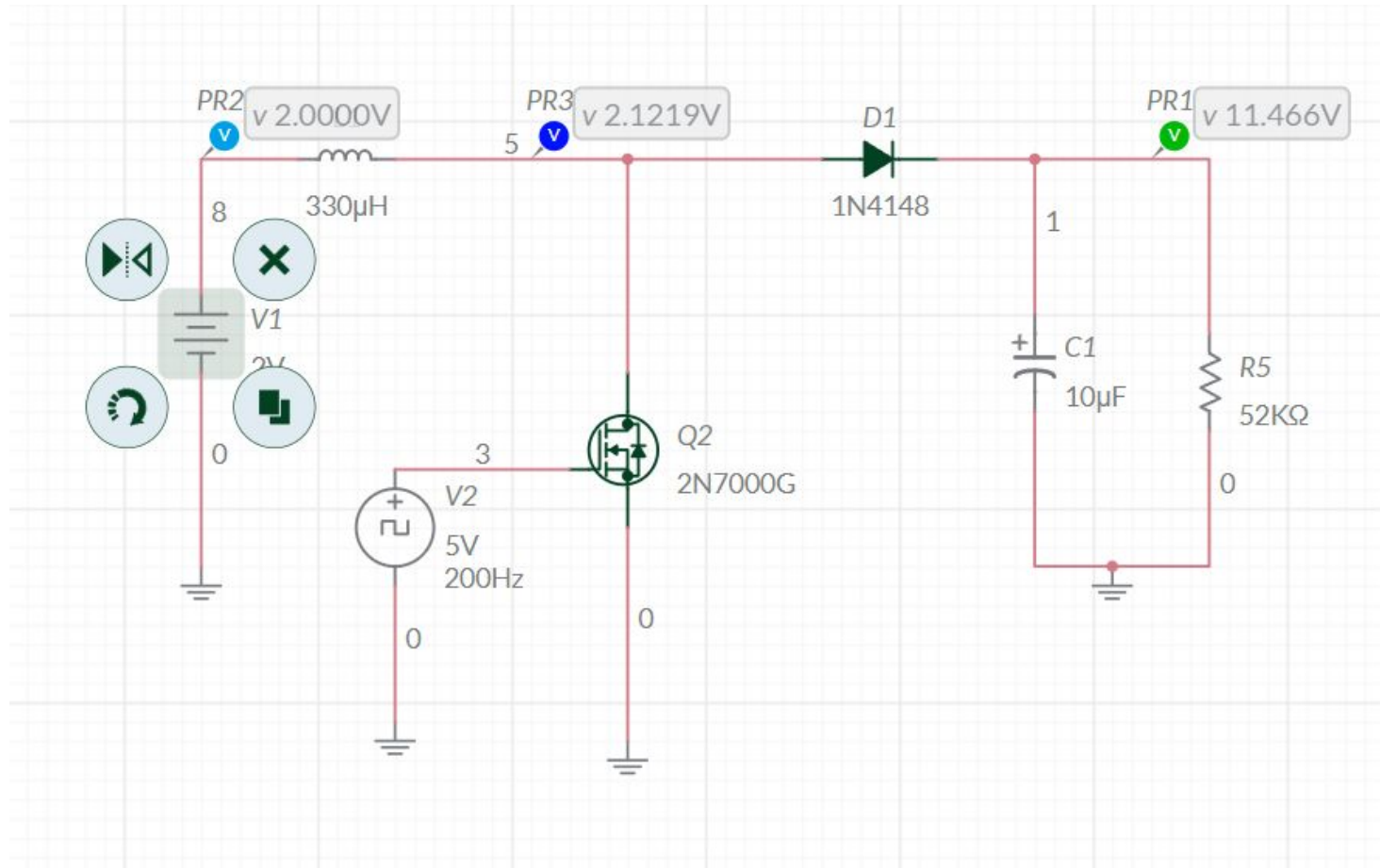

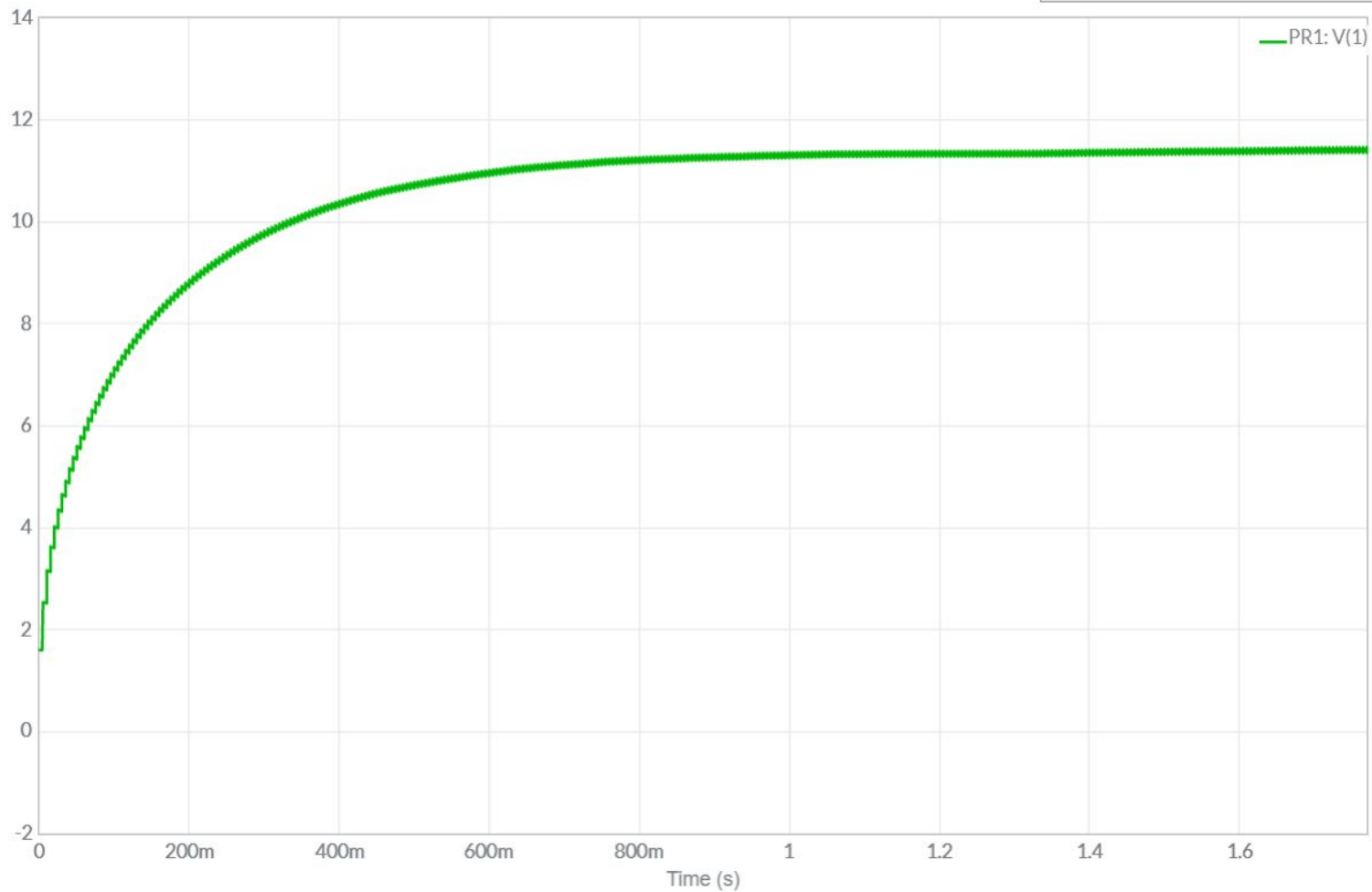As most of the papers we being able to produce a maximum voltage of 2V so I have given 2V as input



Output Graph

I have consulted these two papers to make modifications in the DC-DC boost converter

See discussions, stats, and author profiles for this publication at: <https://www.researchgate.net/publication/3322892>


Feedforward control of DC-DC PWM boost converter

**Electromagnetic Energy Harvesting Circuit with Feedforward and Feedback**

**DC-DC PWM Boost Converter for Vibration Power Generator System**


Boost converter with feedforward



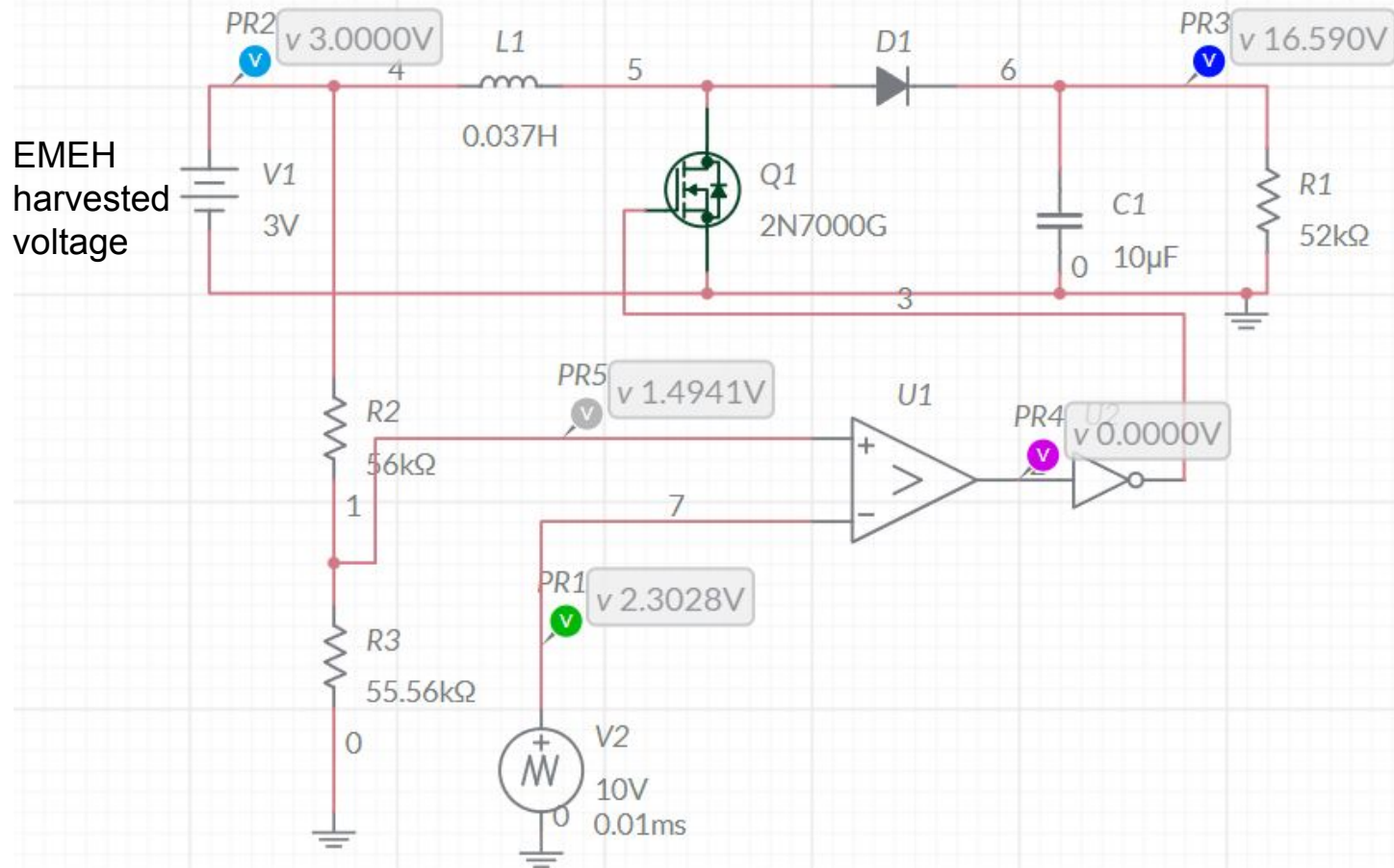

DC-DC boost converter with feedforward circuit

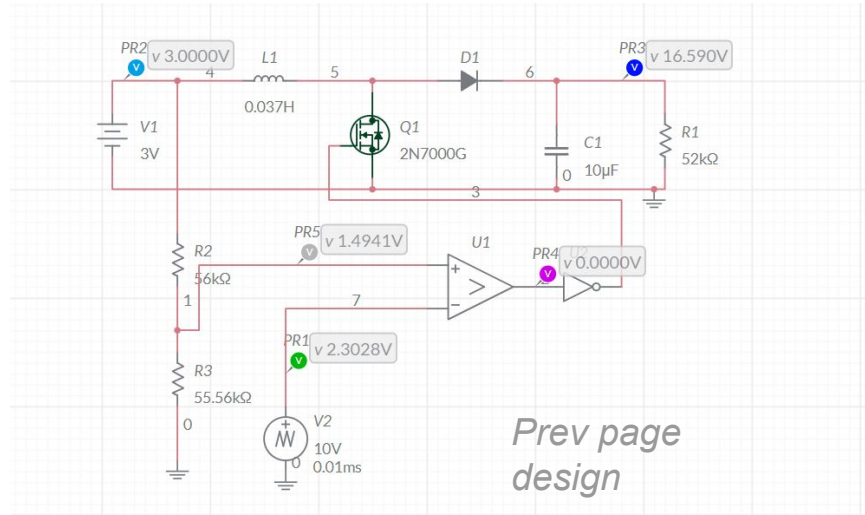
In PWM dc-dc power converters operated in CCM and without any control, the dc output voltage is almost independent of the output current (or load resistance), but is directly proportional to the dc input voltage. Therefore, it is difficult to achieve good line regulation in these converters. So we will introduce a feed forward circuit.



$$V_O = \frac{1}{1-D} V_I \rightarrow V_O = \frac{V_{Tm}}{\alpha} = \left( \frac{R_1}{R_2} + 1 \right) V_{Tm}.$$

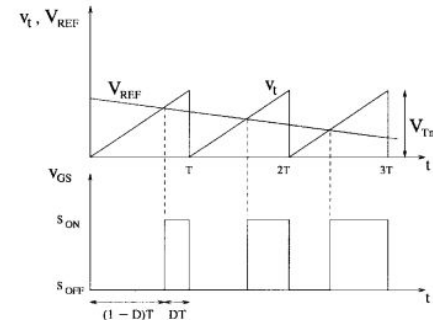
**Vo becoming independent of Vi**

When the reference voltage at the comparator inverting input is higher than the sawtooth voltage at the noninverting input, the gate-to-source voltage goes low, turning the power transistor OFF. On the other hand, when the reference voltage is lower than the sawtooth voltage, the voltage goes high, turning the power transistor ON. Therefore, the on-duty cycle of the power transistor increases as the converter dc input voltage decreases



Boost converter with Amplitude modulated Sawtooth

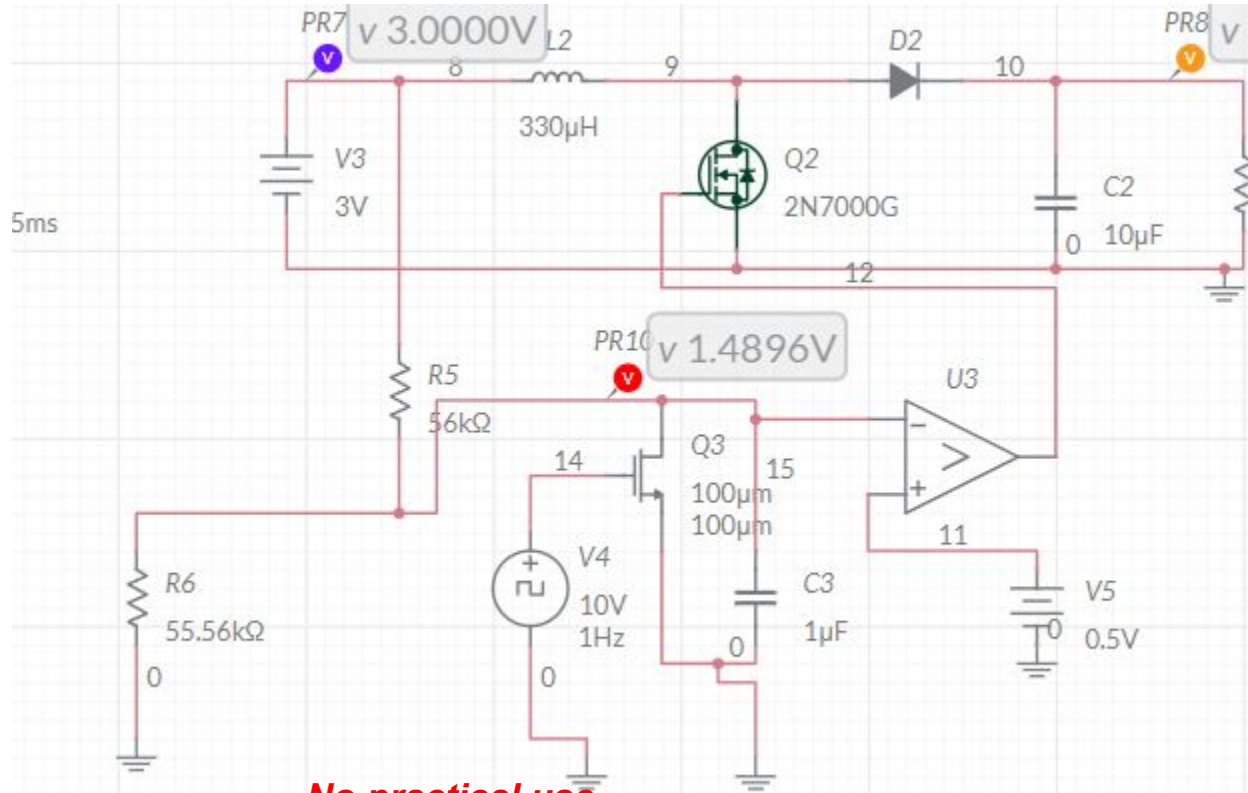We can also change the duty cycle by changing the magnitude of the sawtooth wave and giving a fixed  $v_{ref}$  instead of a variable one as in the previous example



$$V_O = \frac{V_I}{1 - D}$$


$$= \frac{V_I}{1 - \frac{\tau_c V_{REF}}{\alpha T V_I}}.$$


However the output becomes highly dependent on the input so this circuit has no practical values

**No practical use**

Boost converter with both feedforward and feedback


## Boost converter

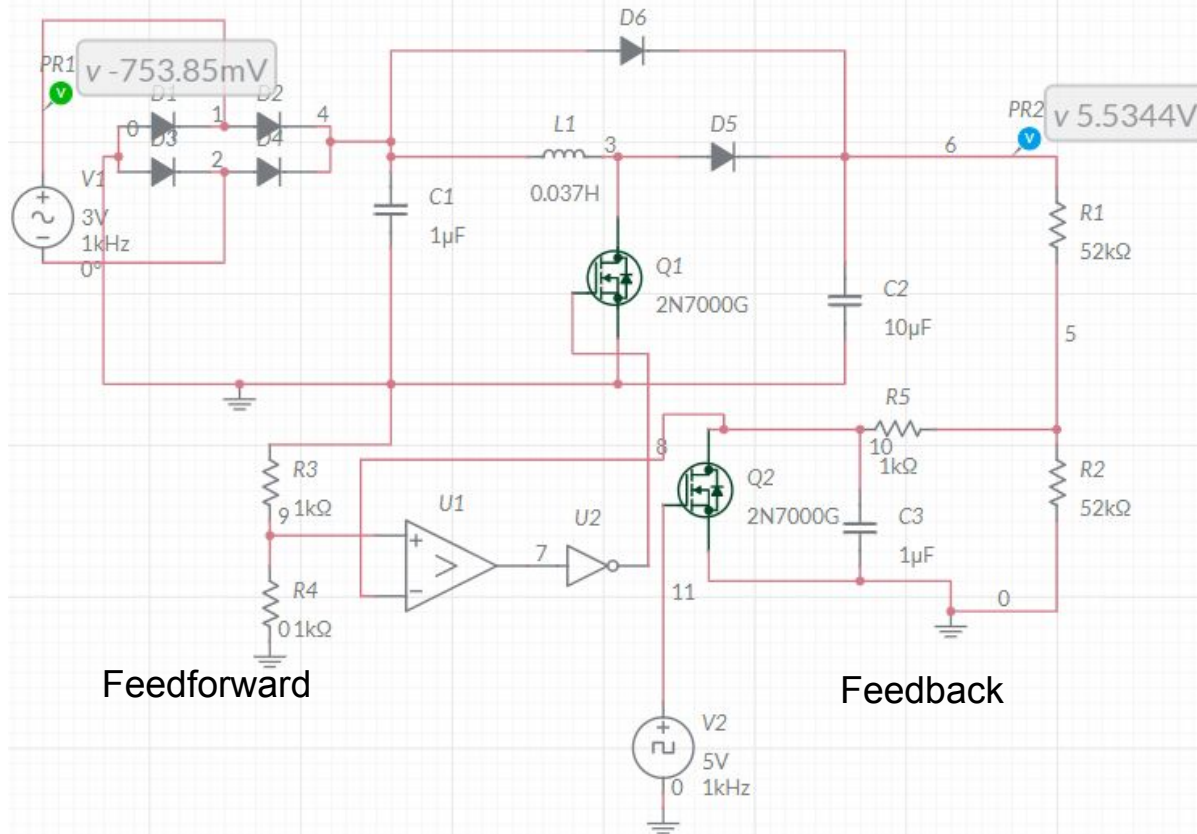

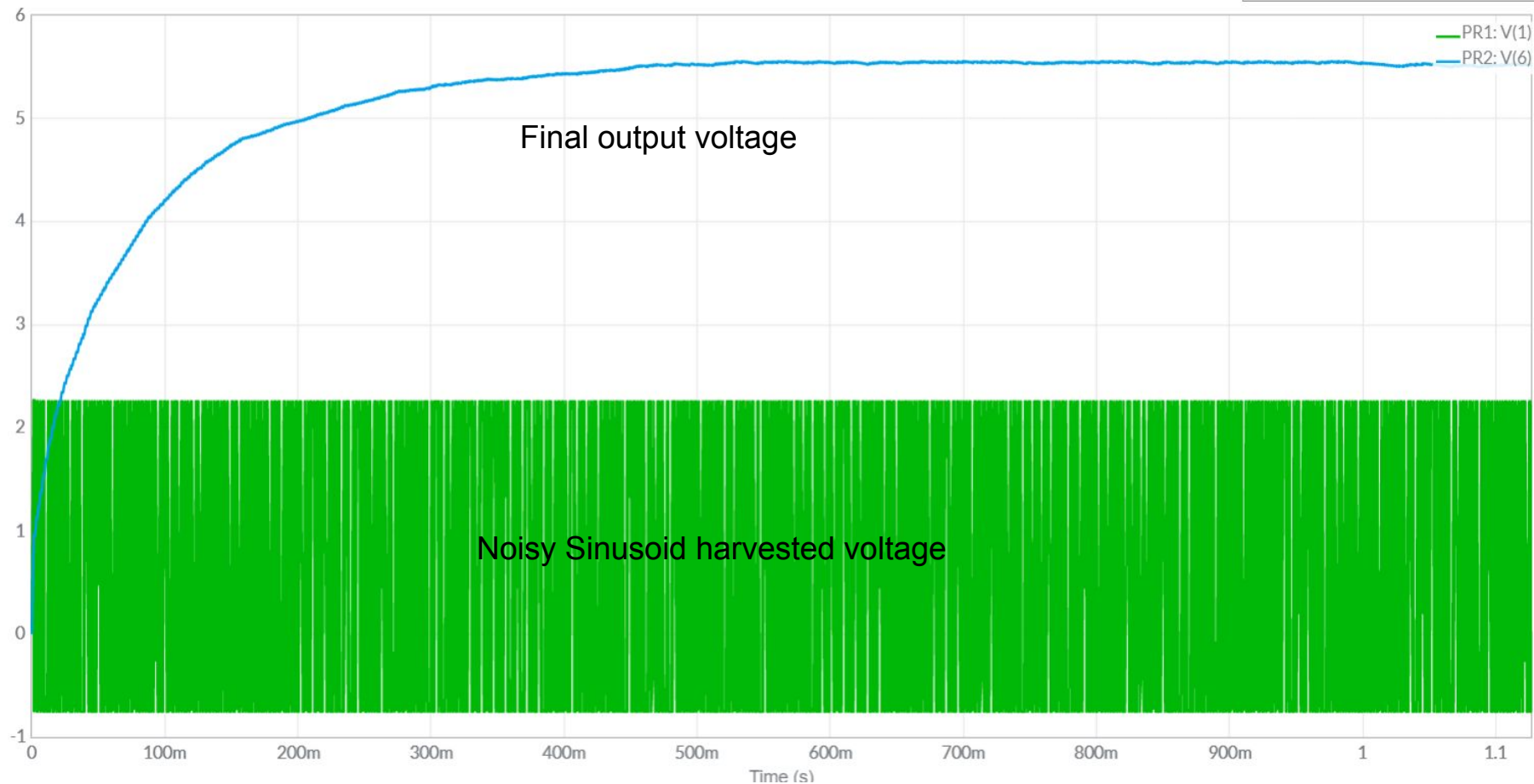


Dual polarity Boost Converter



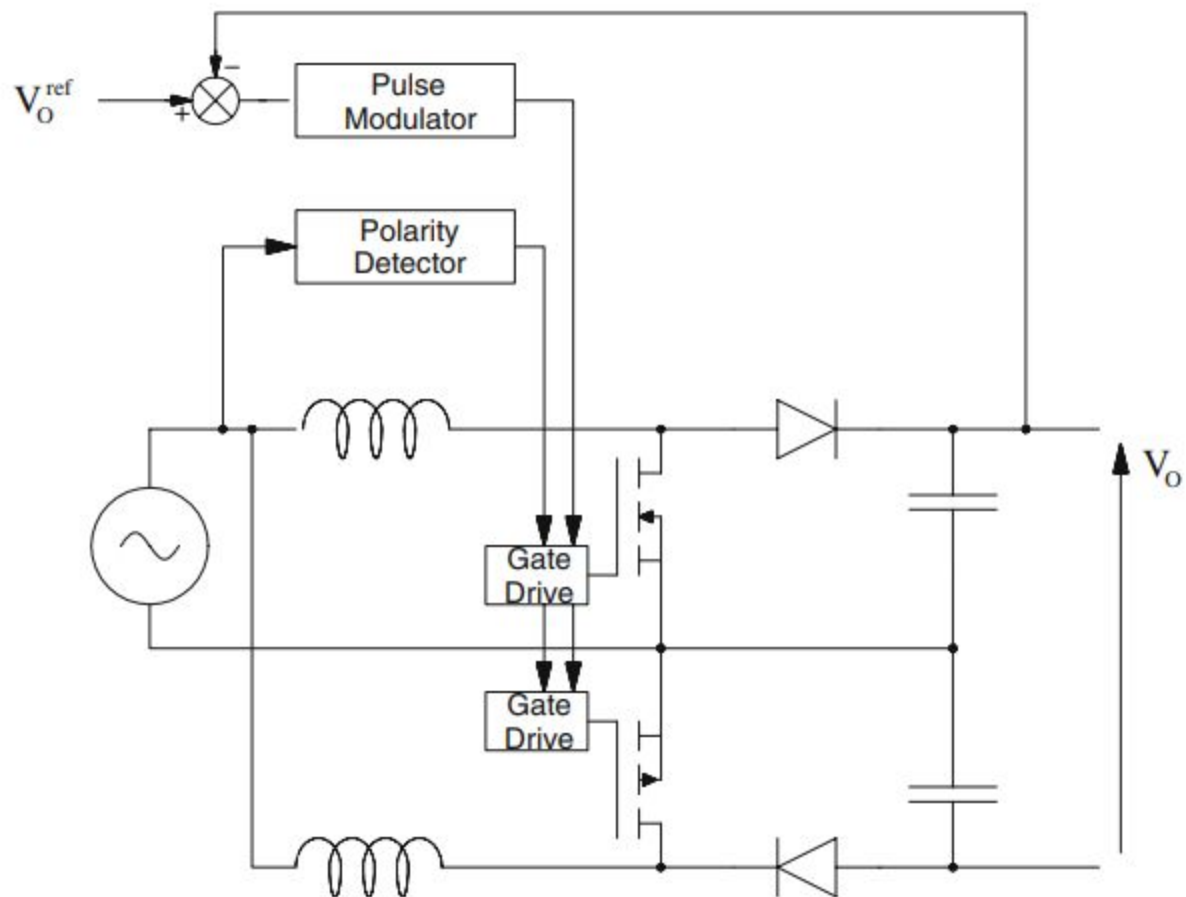


Design proposed in a  
paper

Isolated and Non isolated DC - DC converters

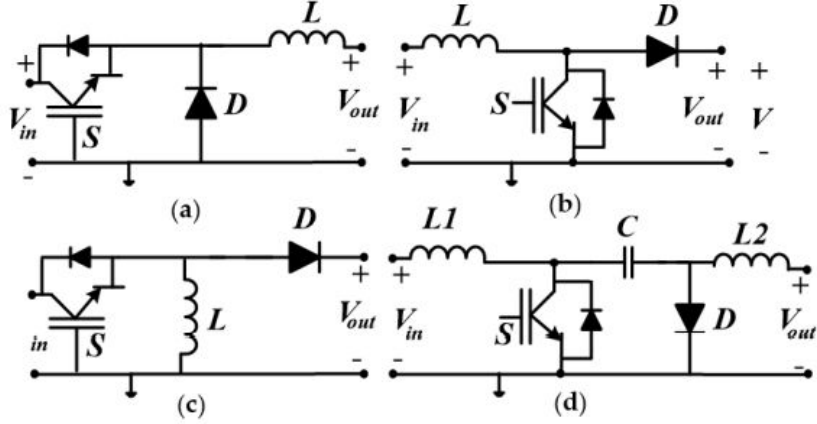

**Figure 30.** Numerous conventional non-isolated DC-DC converters: (a) buck, (b) boost, (c) buck-boost, and (d) Cuk [134].

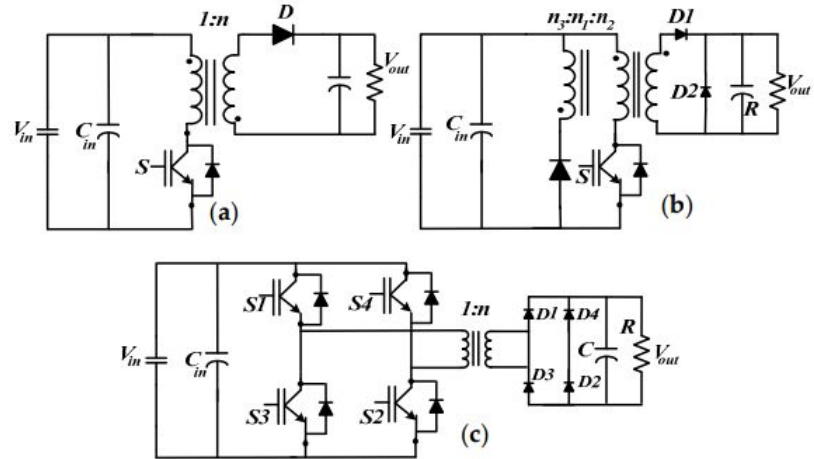

**Figure 31.** Isolated DC-DC converter: (a) flyback converter, (b) forward converter, and (c) full-bridge converter [134].